

Optical front-ends for USRP radios

H. Boeglen¹, S. Joumessi², S. Sahuguède², P. Combeau¹, D. Sauveron² and A. Julien-Vergonjanne²

¹XLIM Lab, UMR CNRS 6172, Université de Poitiers, France ²XLIM Lab, UMR CNRS 6172, Université de Limoges, France

French GNU Radio Days, Lyon

- 1 Introduction
- 2 Design of 10MHz IR frontends for USRP radios
- 3 Demonstration: IR car audio transmission system
- 4 Conclusion and future work

- 1 Introduction
- 2 -
- 3 -
- 4 -

1. Introduction

□ Infrared (IR) optical communication is a good candidate for indoor wireless communications:

- → large bandwidth available
- → confined to the room where they are operated: advantage for secure communications
- → less influence on the human body than RF technologies
- We are involved in the Aircraft Light Communication (ALC) Cleansky2 H2020 project:

→Goal: design of a secured and performant wireless connection based on light (LiFi) for Electronic Flight Bag (EFB), headset and other pilot connected devices.

→Need for a flexible IR transceiver to help for the design of efficient transmission schemes



Software Defined Radio provides great flexibility for evaluating different optical wireless schemes. We therefore decided to design infrared optical front-ends for Ettus USRP radios.

2 - Design of 10MHz IR frontends for USRP radios

3 -

1 -


4 -

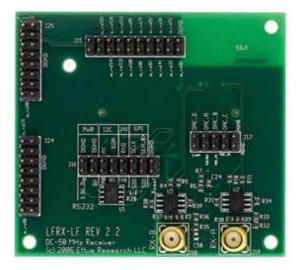2. Design of 10MHz IR frontends for USRP radios

Design choices

□ A transmission bandwidth of 10MHz
□ An IR link works in baseband with 0Hz (LED and Photodiode perform up/down conversion to the IR wavelength)
→ LFTX and LFRX daugtherboards cover these needs





- → 0-30MHz bandwidth
- **→** 83€

→ An USRP N210 can be fitted by 1 LFTX and 1 LFRX (full duplex)

The transmitter


□ An infrared LED is current-driven




- → LFTX voltage output (-1/+1V) has to be converted to 0-100mA
- Classical voltage to current converter structure with an high speed, high current operational amplifier (op amp)
- → Only 6V output from USRP is able to source this current.
- → An IR LED has a forward voltage of 1.7V thus we can connect up to 3 LEDs in series

The transmitter


□ Schematic and designed board

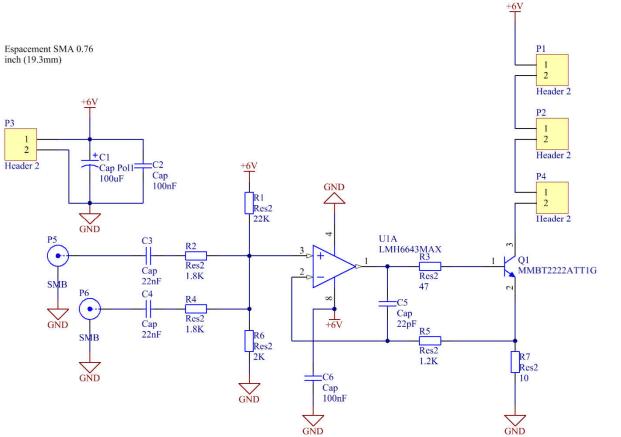

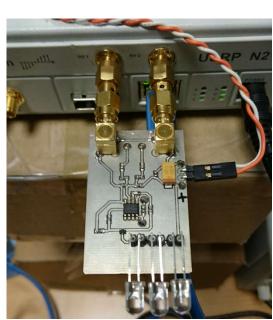

The receiver

□ A PIN photodiode is used

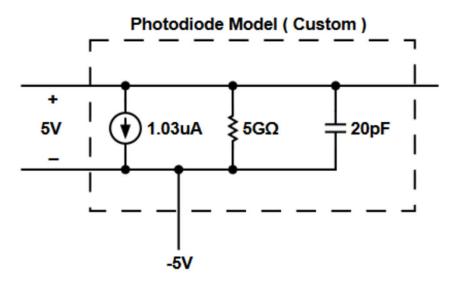


→ Converts light energy into a current

- → A very low current (10uA) has to be converted to voltage
- → The classical circuit is built around a Transimpedance Amplifier (TIA)
- → There are specific op amps for this application (expensive \approx 10€)
 - → Low input bias currents (JFET preamplifiers)
 - → Very high gain-product bandwidth (typically over 1GHz)

The receiver

□ Using Analog Devices online Wizard:

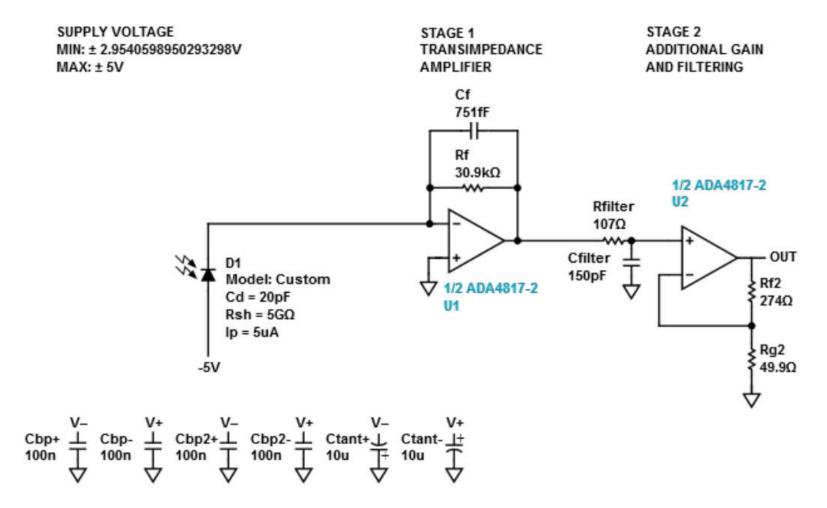


→ Extreme care has to be taken when routing the design (751fF, smd)

The receiver

□ Reducing costs:

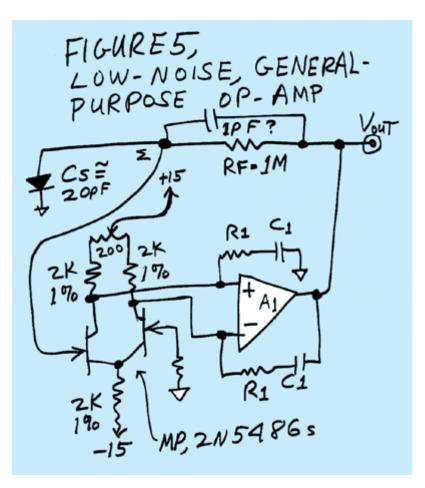→ HF JFET transistor in front of a classical op amp (less than 1€)




- 2 -
- 3 Demonstration: IR car audio transmission system
- 4 -

1 –

3. Demonstration: IR car audio transmission system

IR car audio entertainment system

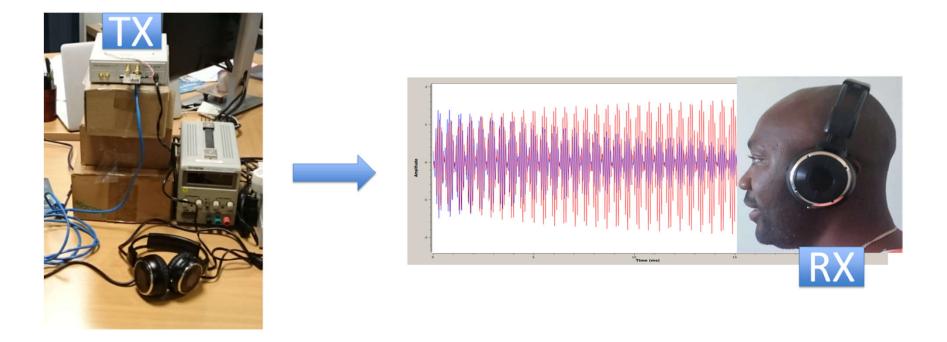


→ Stereo audio signal on two FM modulated carrier frequencies at 2.3MHz and 2.8MHz

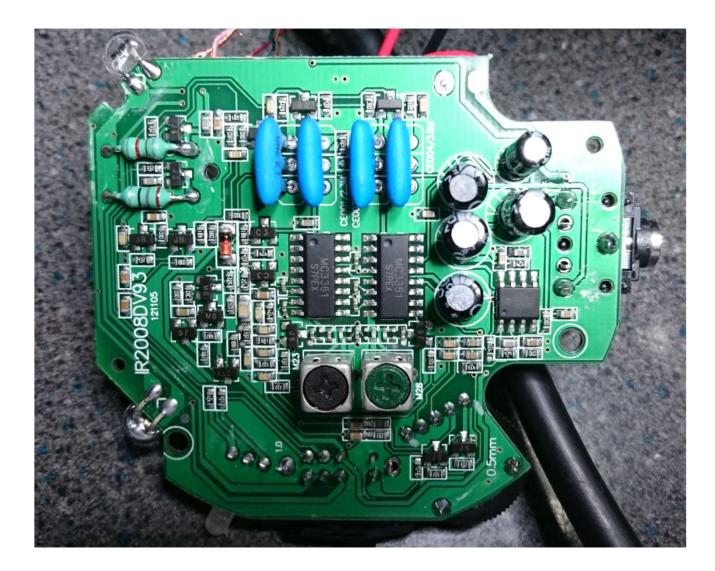3. Demonstration: IR car audio transmission system

IR car audio entertainment system


□ Inside the headphones (10€ on the Internet):



3. Demonstration: IR car audio transmission system

IR car audio entertainment system

GNU Radio flowgraph:

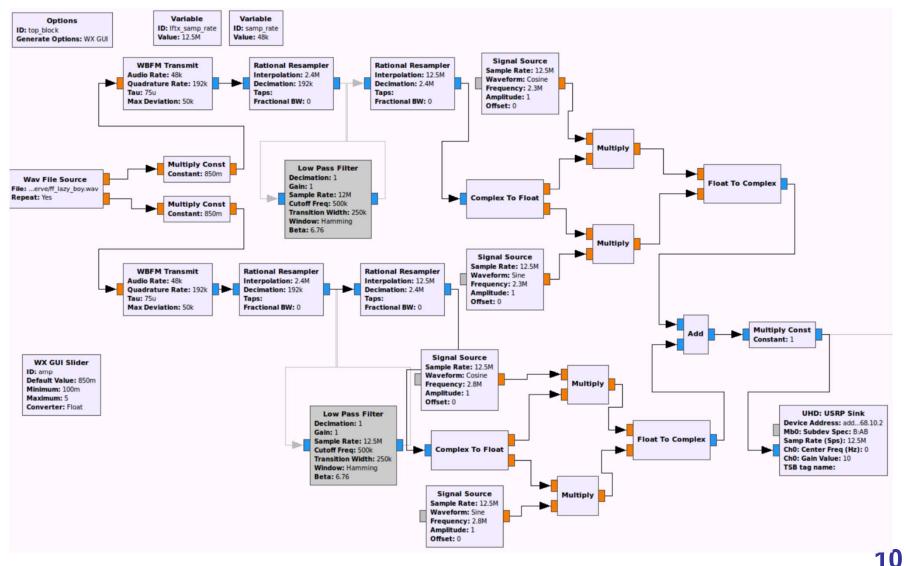

1 -



2 3 4 - Conclusion and future work

Ettus Research offers a large range of RF daugtherboards

However the daughterboard interface is quite generic
easy to develop a custom board

This permits to enter the GNU Radio world and its huge range of librairies

□Our IR boards cost less than 50€.

Future work: design of a configurable AGC for the IR receiver.

THANK YOU!

QUESTIONS?



References

[1] <u>https://www.ettus.com/</u>

[2] A. Julien-Vergonjanne, S. Sahuguède, L. Chevalier, (2016) Optical Wireless Body Area Networks for Healthcare Applications, In: Uysal M., Capsoni C., Ghassemlooy Z., Boucouvalas A., Udvary E. (eds) Optical Wireless Communications. Signals and Communication Technology. Springer, Cham

[3] J. Ardizzoni, A Practical Guide to HighSpeed Printed-Circuit-Board Layout, Analog Dialogue, Vol. 39, Sep. 2005.

[4] J. Greame, "Photodiode amplifiers, op amp solutions", Mc Graw-Hill, 1996.